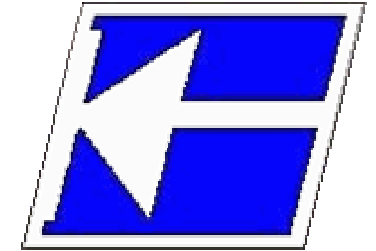


**Centro Federal de Educação Tecnológica de Santa Catarina**

**Departamento de Eletrônica**

**Eletrônica Básica e Projetos Eletrônicos**



**Diodos**

**e**

**Análise de circuitos simples com diodos**

**Clóvis Antônio Petry, professor.**

**Florianópolis, março de 2007.**



# Nesta aula

---

## **Seqüência de conteúdos:**

1. Características dos diodos;
2. Análise de circuitos com diodos;
3. Aplicações simples.

# Bibliografia

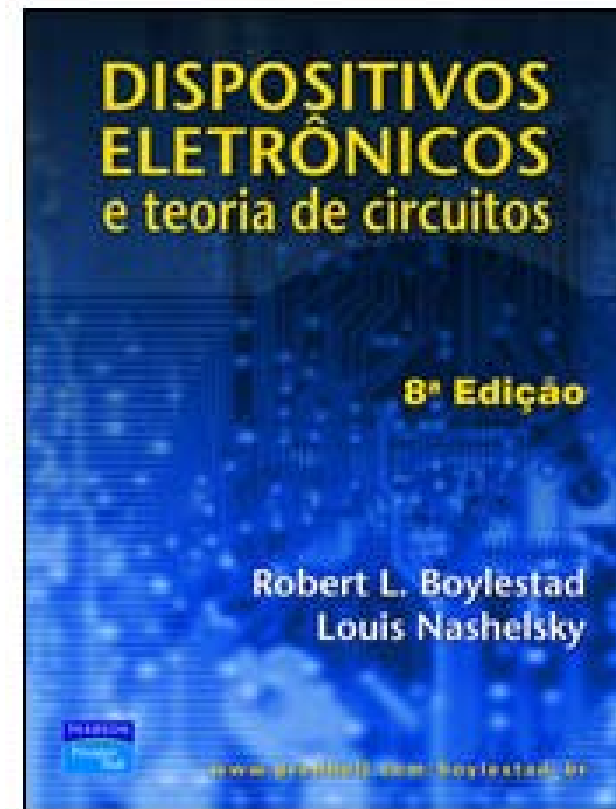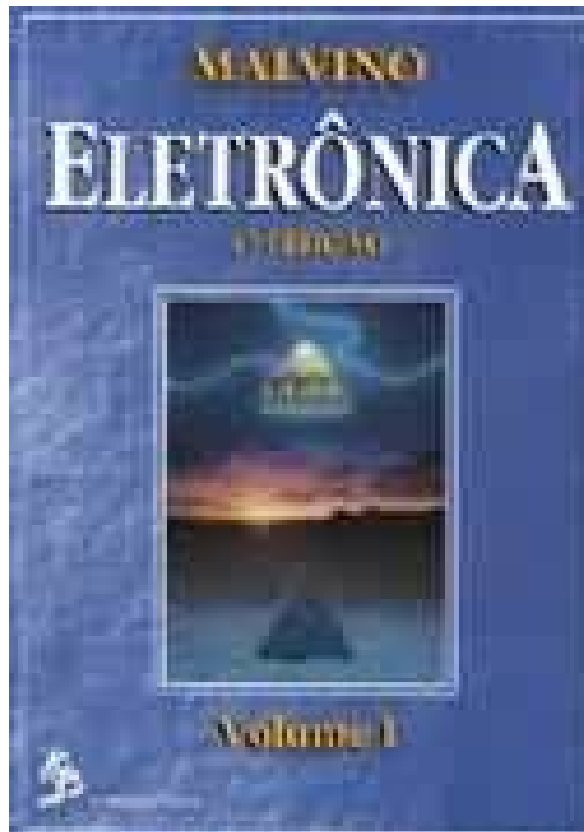

# Características dos diodos

**As principais características (grandezas) são:**

1. Corrente máxima direta ( $I_F$  ou  $I_o$ );
2. Tensão de ruptura reversa:
  - VRRM = Tensão de pico inverso repetitivo;
  - VRWM = Tensão de pico inverso de trabalho;
  - VR = Tensão de bloqueio CC.
3. Queda de tensão direta ( $v_F$ );
4. Corrente reversa máxima ( $I_R$ ).
5. Entre outras ....

# Características dos diodos

**VISHAY**

**1N4001 thru 1N4007**  
Vishay Semiconductors  
formerly General Semiconductor

**General Purpose Plastic Rectifier**

Reverse Voltage  
50 to 1000V  
Forward Current 1.0A

**Features**

- Plastic package has Underwriters Laboratories Flammability Classification 94V-0
- Construction utilizes void-free molded plastic technique
- Low reverse leakage
- High forward surge capability
- High temperature soldering guaranteed: 350°C/10 seconds, 0.375" (9.5mm) lead length, 5 lbs. (2.3kg) tension

**Mechanical Data**

Case: JEDEC DO-204AL, molded plastic body  
Terminals: Plated axial leads, solderable per MIL-STD-750, Method 2026  
Polarity: Color band denotes cathode and  
Mounting Position: Any  
Weight: 0.012 oz., 0.3 g

Dimensions in inches and (millimeters)

## Maximum Ratings & Thermal Characteristics

Parameter	Symb.	Ratings at 25°C ambient temperature unless otherwise specified.							Unit
		1N 4001	1N 4002	1N 4003	1N 4004	1N 4005	1N 4006	1N 4007	
Maximum repetitive peak reverse voltage	V <sub>RRM</sub>	50	100	200	400	600	800	1000	V
* Maximum RMS voltage	V <sub>RMS</sub>	35	70	140	280	420	560	700	V
* Maximum DC blocking voltage	V <sub>DC</sub>	50	100	200	400	600	800	1000	V
* Maximum average forward rectified current 0.375" (9.5mm) lead length at T <sub>A</sub> = 75°C	I <sub>F(AV)</sub>	1.0							A
* Peak forward surge current 8.3ms single half sine-wave superimposed on rated load (JEDEC Method) T <sub>A</sub> = 75°C	I <sub>FSM</sub>	30							A
* Maximum full load reverse current, full cycle average 0.375" (9.5mm) lead length T <sub>L</sub> = 75°C	I <sub>R(AV)</sub>	30							µA
Typical thermal resistance <sup>(1)</sup>	R <sub>θJA</sub> R <sub>θAL</sub>	50 25							°C/W
* Maximum DC blocking voltage temperature	T <sub>A</sub>	+150							V
* Operating junction and storage temperature range	T <sub>J</sub> , T <sub>STG</sub>	-50 to +175							°C

## Electrical Characteristics

Ratings at 25°C ambient temperature unless otherwise specified.				
Maximum instantaneous forward voltage at 1.0A	V <sub>F</sub>	1.1		V
* Maximum DC reverse current at rated DC blocking voltage T <sub>A</sub> = 25°C T <sub>A</sub> = 125°C	I <sub>R</sub>	5.0 50		µA
Typical junction capacitance at 4.0V, 1MHz	C <sub>J</sub>	15		pF

Note: (1) Thermal resistance from junction to ambient at 0.375" (9.5mm) lead length, P.C.B. mounted. \*JEDEC registered value

Bulletin PD-20731 rev. C 12/05

International  
**IR** Rectifier

**MUR820**  
**MURB820**  
**MURB820-1**

## Ultrafast Rectifier

### Features

- Ultrafast Recovery Time
- Low Forward Voltage Drop
- Low Leakage Current
- 175°C Operating Junction Temperature

t<sub>r</sub> = 25ns  
I<sub>F(AV)</sub> = 8Amp  
V<sub>R</sub> = 200V

### Description/Applications

International Rectifier's MUR... series are the state of the art Ultra fast recovery rectifiers specifically designed with optimized performance of forward voltage drop and ultra fast recovery time. The planar structure and the platinum doped life time control, guarantee the best overall performance, ruggedness and reliability characteristics. These devices are intended for use in the output rectifier stage of SMPS, UPS, DC-DC converters as well as free-wheeling diode in low voltage inverters and chopper motor drives. Their extremely optimized stored charge and low recovery current minimize the switching losses and reduce over dissipation in the switching element and snubbers.


### Absolute Maximum Ratings

Parameters	Max.	Units
V <sub>RRM</sub> Peak Repetitive Peak Reverse Voltage	200	V
I <sub>F(AV)</sub> Average Rectified Forward Current Total Device, (Rated V <sub>F</sub> ), T <sub>C</sub> = 150°C	9	A
I <sub>FSM</sub> Non Repetitive Peak Surge Current	100	
I <sub>RM</sub> Peak Repetitive Forward Current (Rated V <sub>R</sub> , Square wave, 50 kHz), T <sub>C</sub> = 150°C	10	
T <sub>J</sub> , T <sub>STG</sub> Operating Junction and Storage Temperature	-55 to 175	°C



**Case Styles**

 TO-220AC	 D <sup>2</sup> PAK	 TO-282
---	---	---


# Características dos diodos

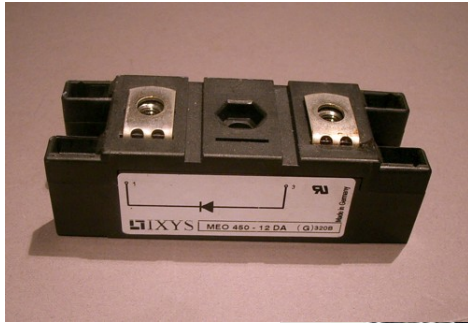

Diodos de potência

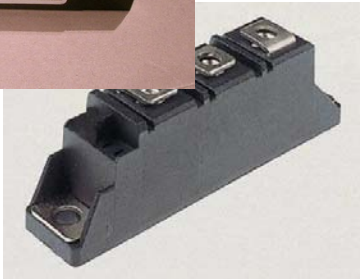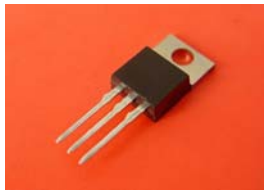



Diodos de sinal

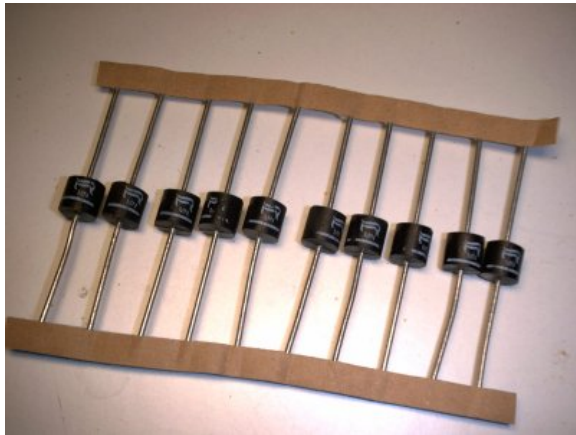


Diodos de uso geral



Circuitos integrados de diodos

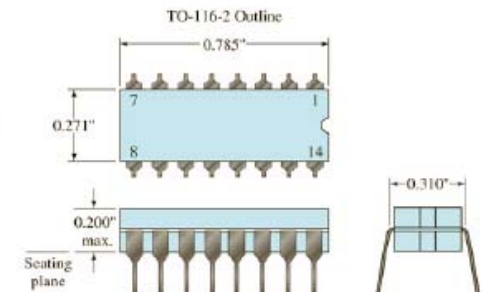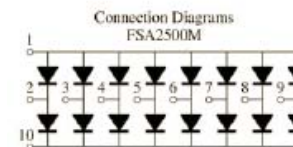


## Análise de circuitos com diodos

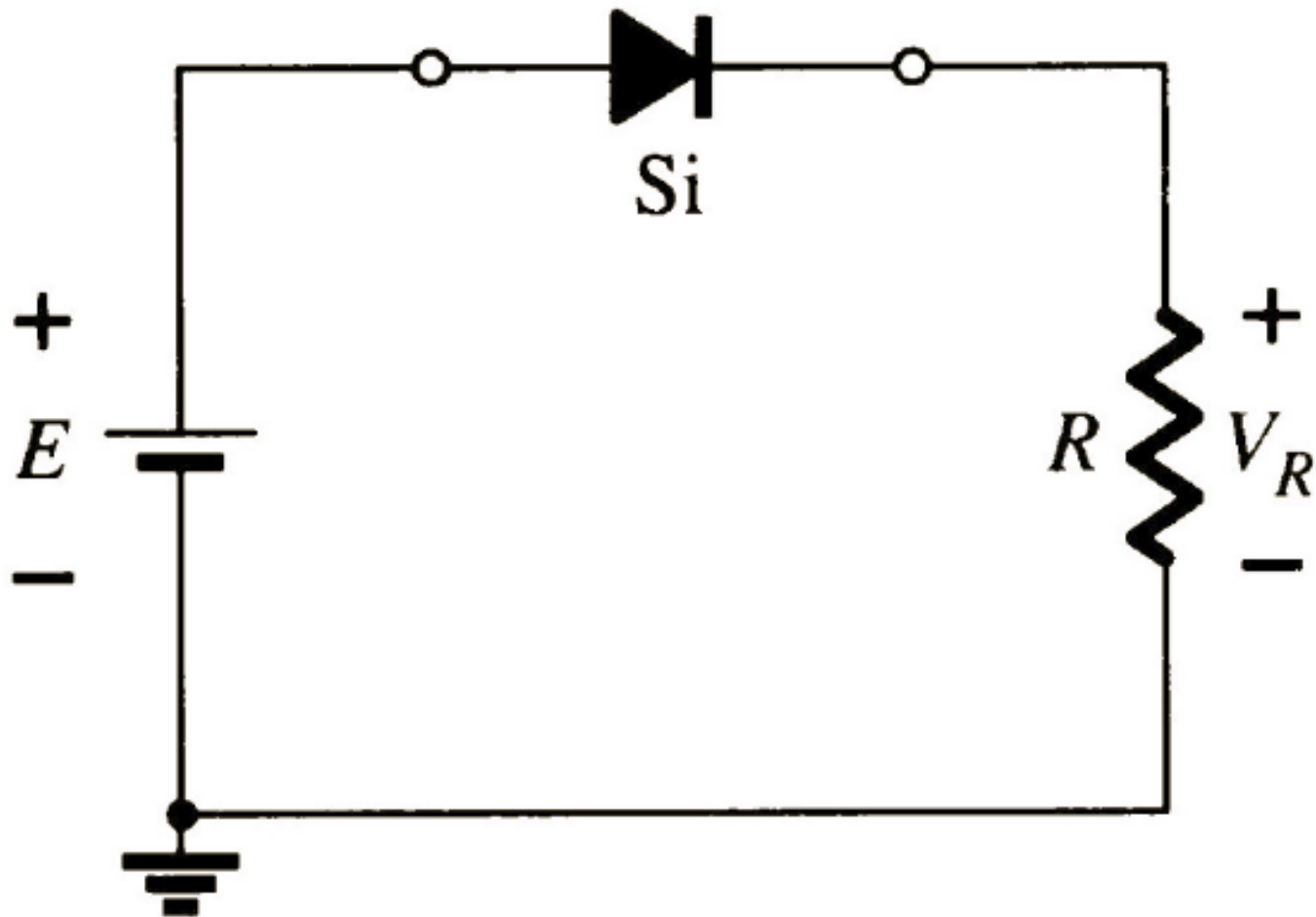

Determine a tensão e a corrente na carga para diversos valores de  $E$  e  $R$ :


- $E = 5 \text{ V}$  e  $R = 1 \text{ k}\Omega$ ;
- $E = 10 \text{ V}$  e  $R = 1 \text{ k}\Omega$ ;
- $E = 10 \text{ V}$  e  $R = 10 \text{ k}\Omega$ .

## Análise de circuitos com diodos

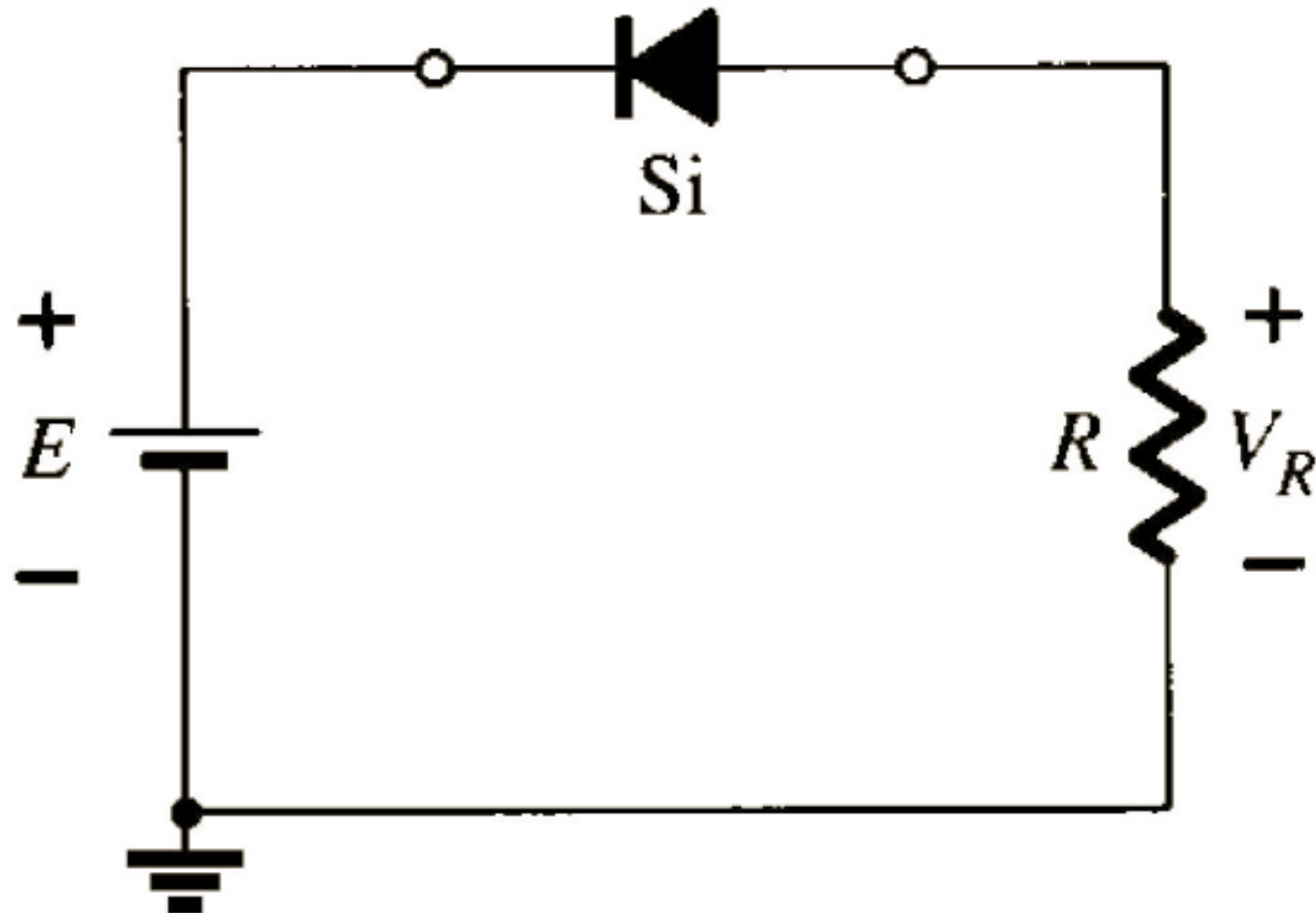


Considerando que o diodo do circuito é o 1N4001, para qual tensão da bateria ( $E$ ) o diodo entrará em condução reversa?

# Análise de circuitos com diodos

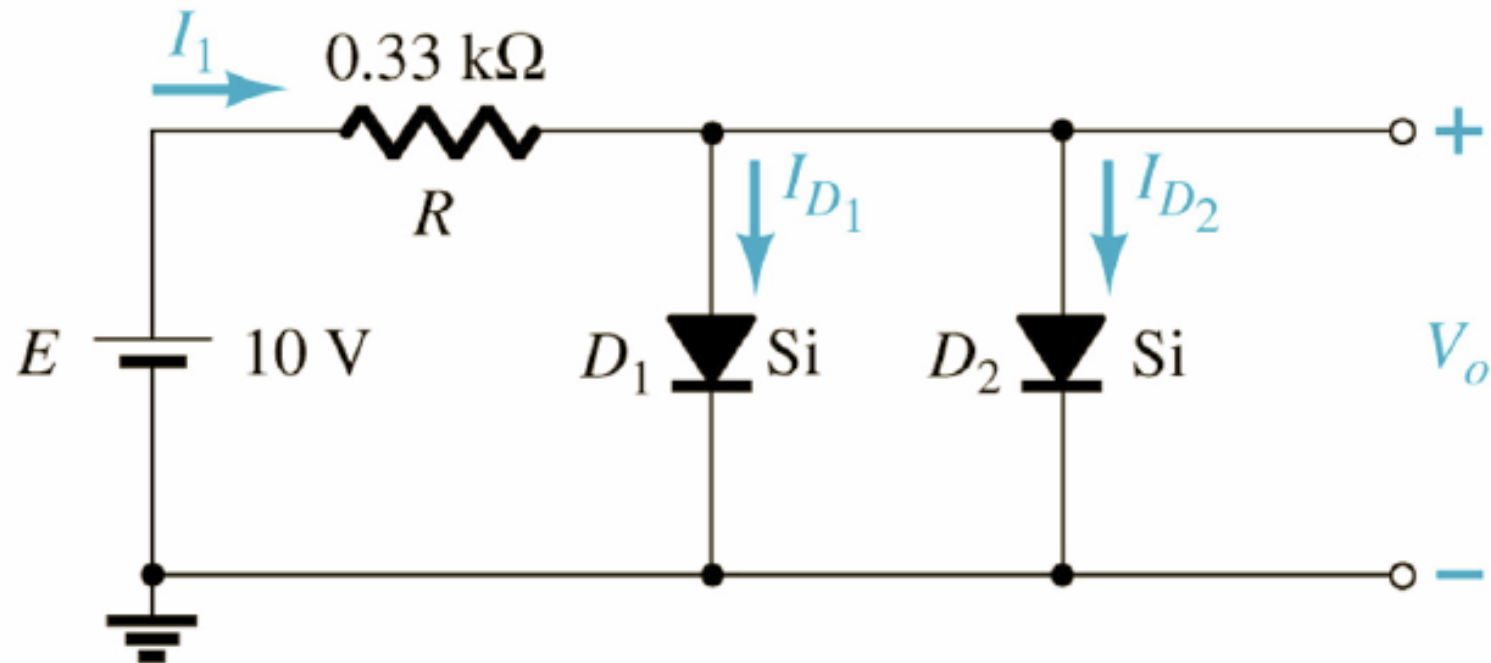


Determine todas as correntes para o circuito acima.

## Análise de circuitos com diodos

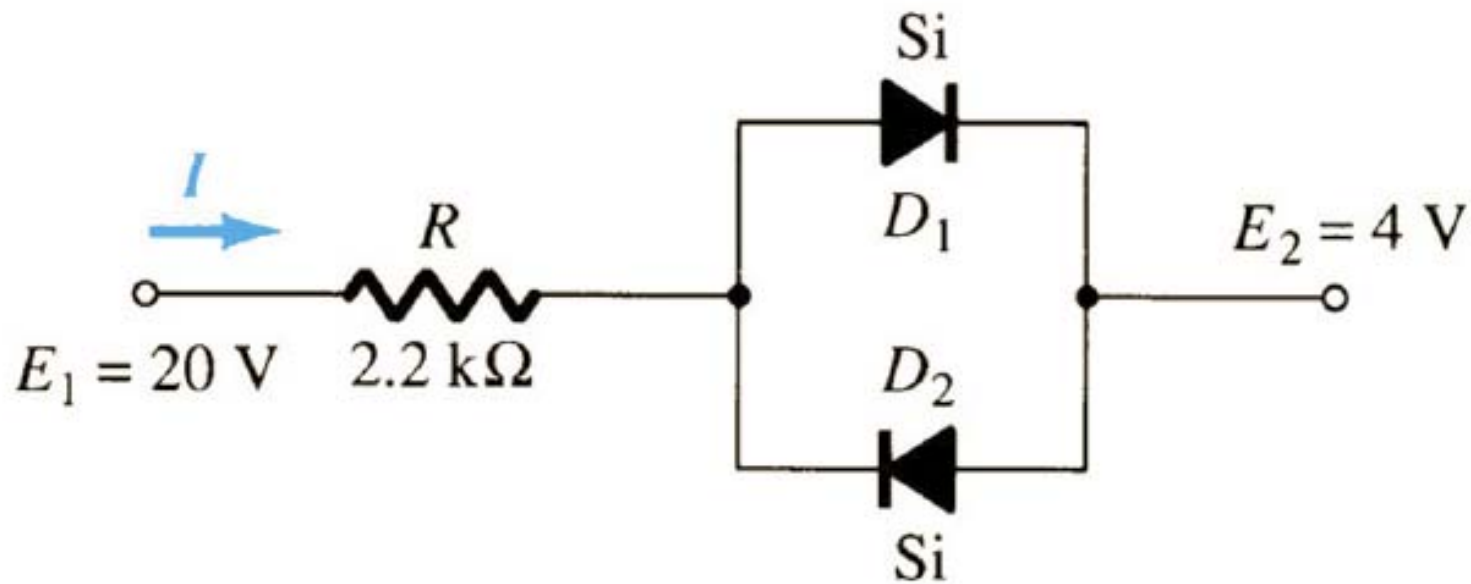

Determine a corrente  $I$  e as correntes nos diodos do circuito acima.


# Análise de circuitos com diodos

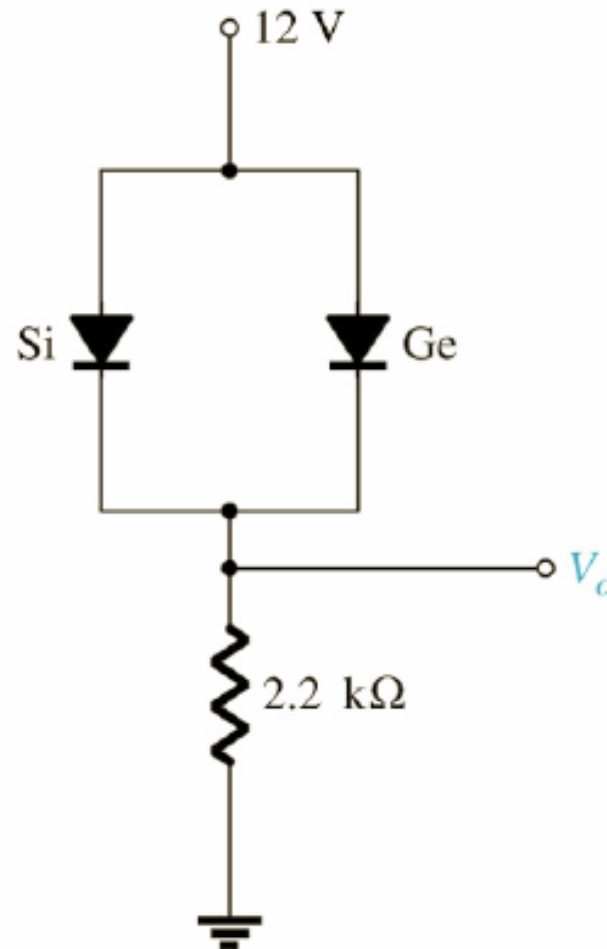

Determine a tensão  $V_o$  e indique o estado dos diodos da figura acima.

# Aplicações simples


Porta lógica OU (or) com diodos:

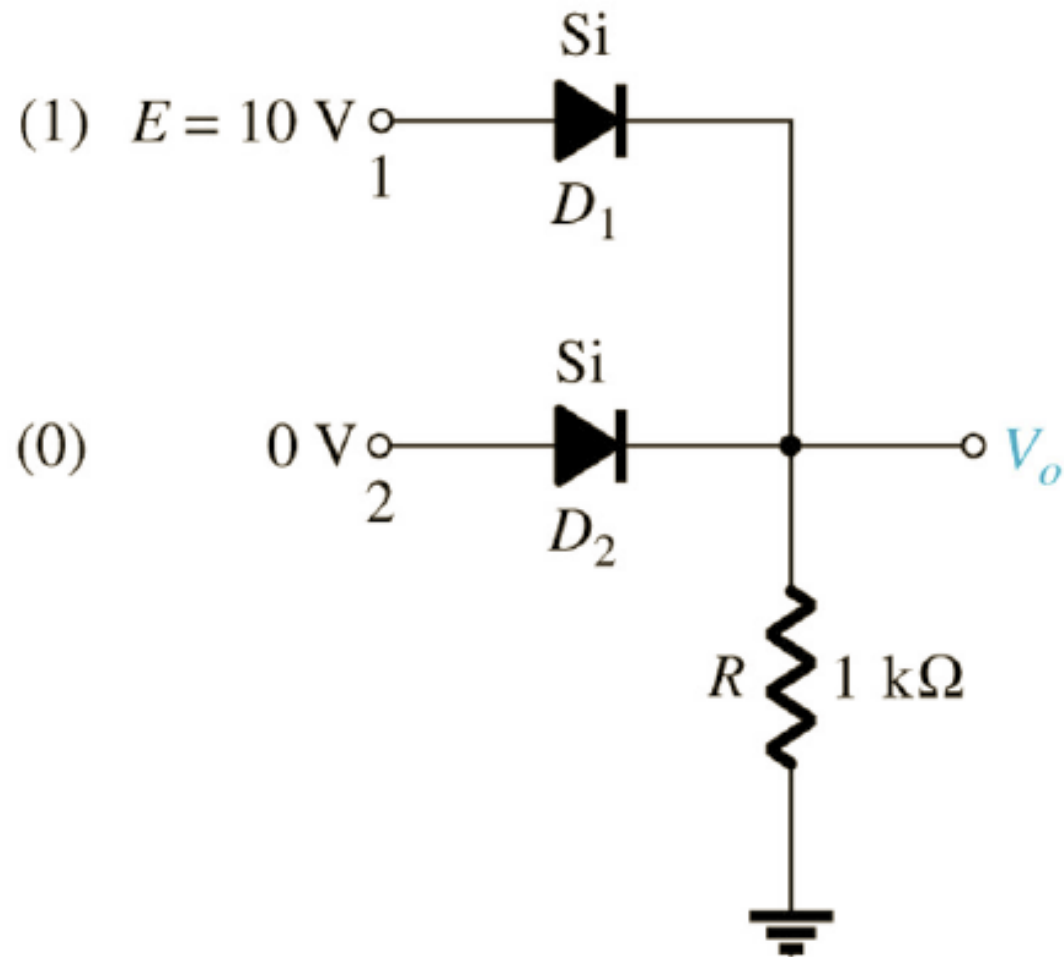

Determine a tensão  $V_o$  e explique o funcionamento do circuito lógico acima.



# Aplicações simples

Porta lógica E (AND) com diodos:

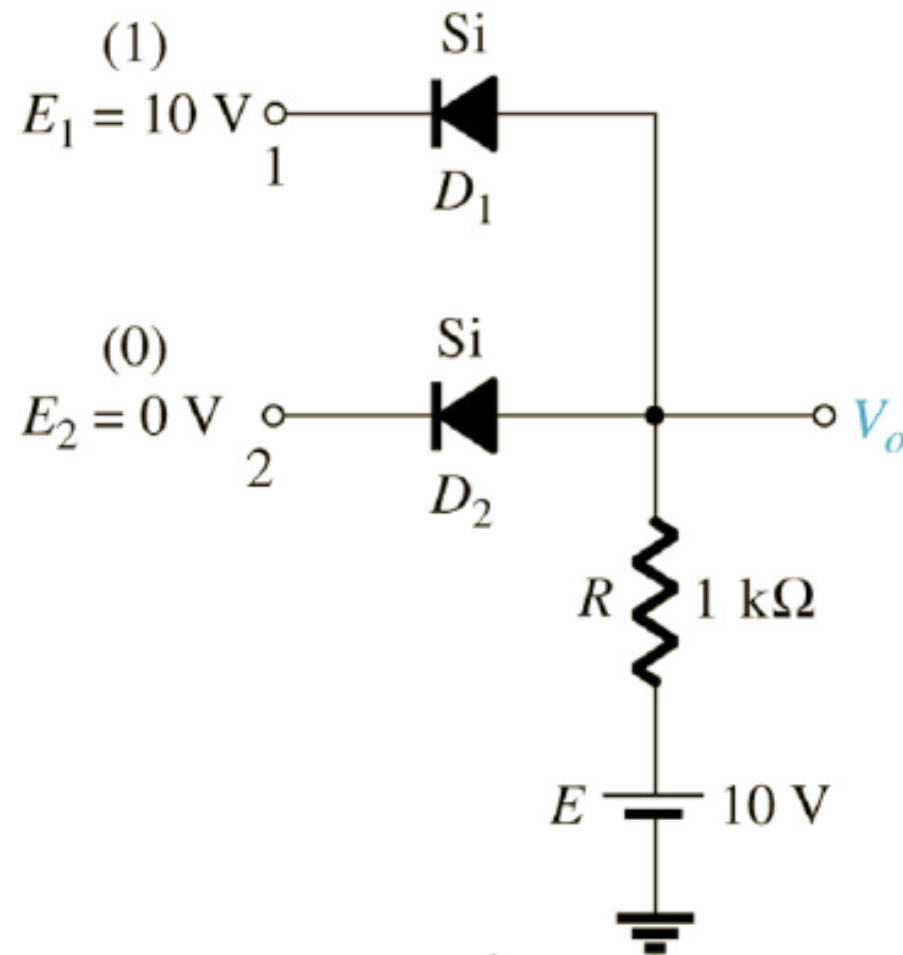



Determine a tensão  $V_o$  e explique o funcionamento do circuito lógico acima.

# Aplicações simples

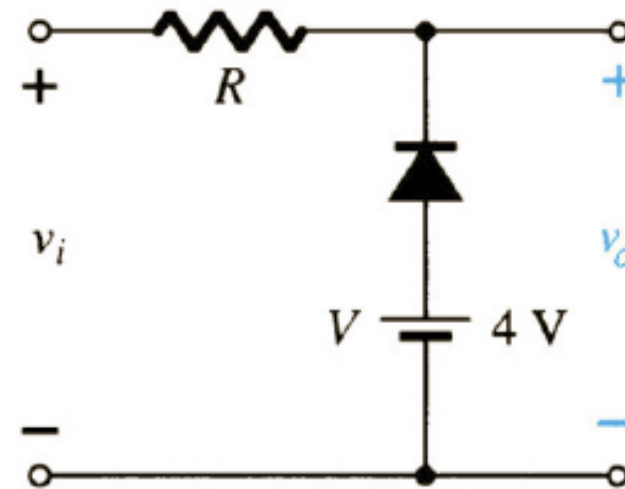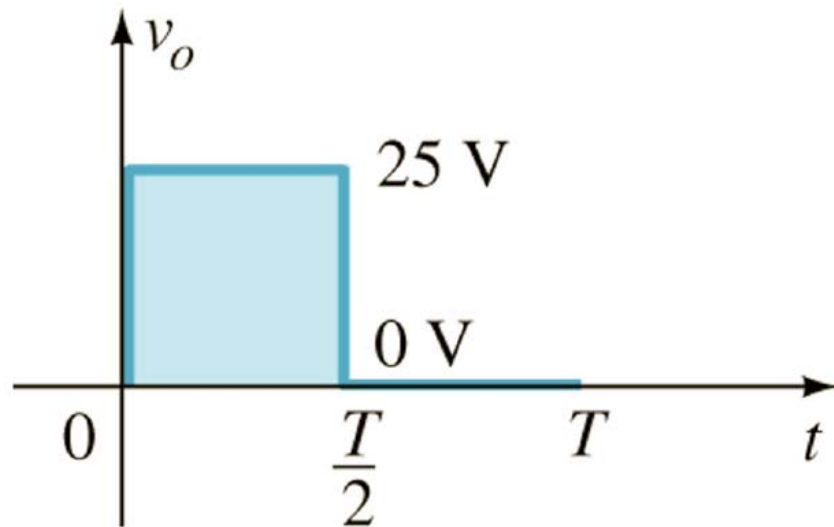



Determine a forma de onda da tensão  $V_o$  para o circuito da figura acima.

# Aplicações simples

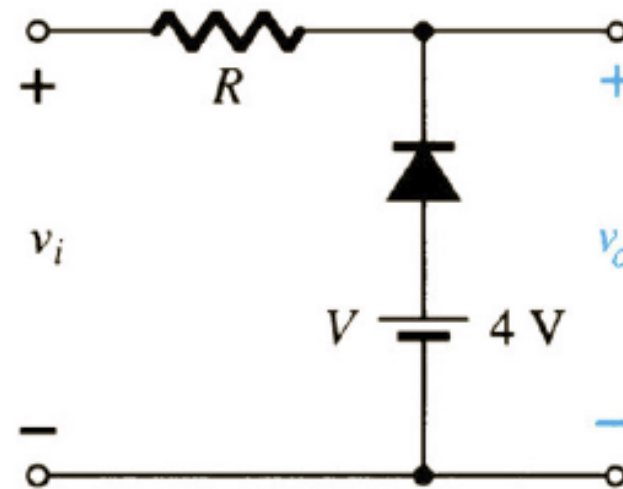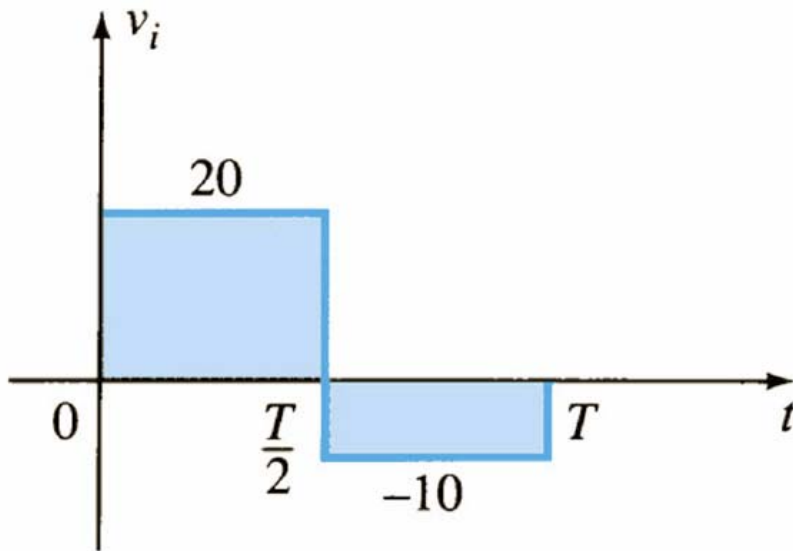



Determine a forma de onda da tensão  $V_o$  para o circuito da figura acima.

# Aplicações simples

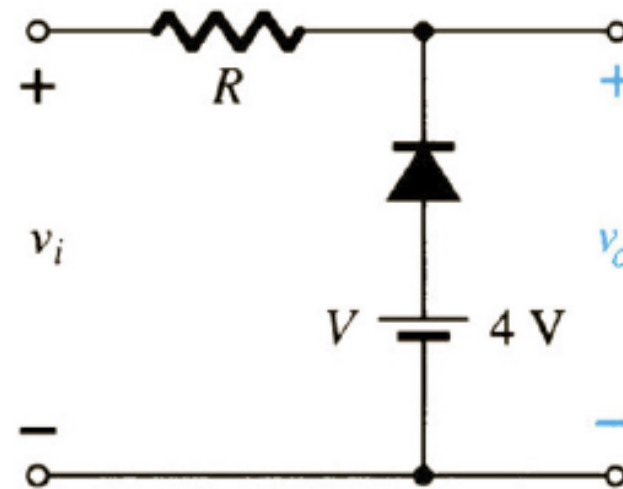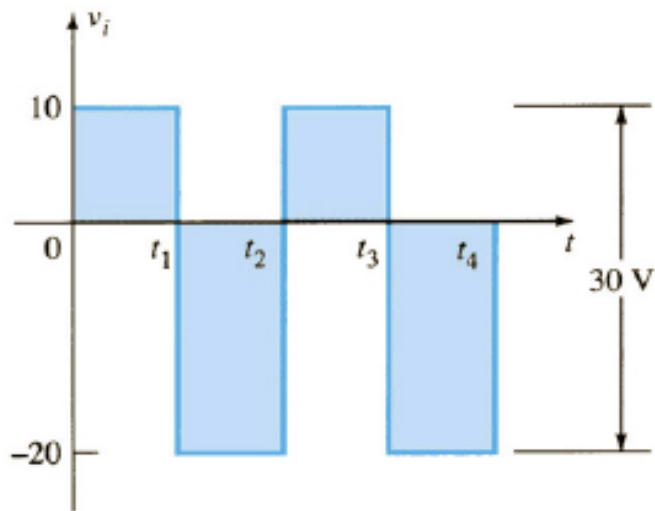


Determine a forma de onda da tensão  $V_o$  para o circuito da figura acima.

# Aplicações simples

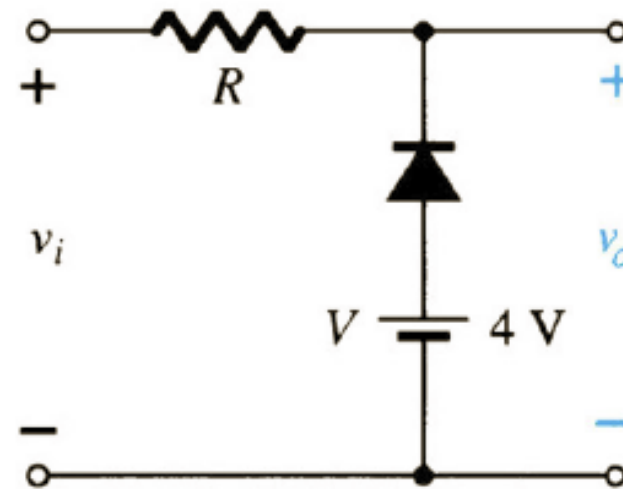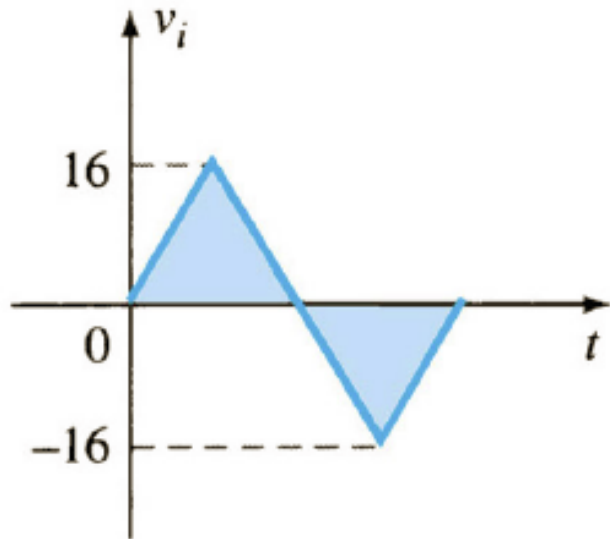


Determine a forma de onda da tensão  $V_o$  para o circuito da figura acima.

## Aplicações simples

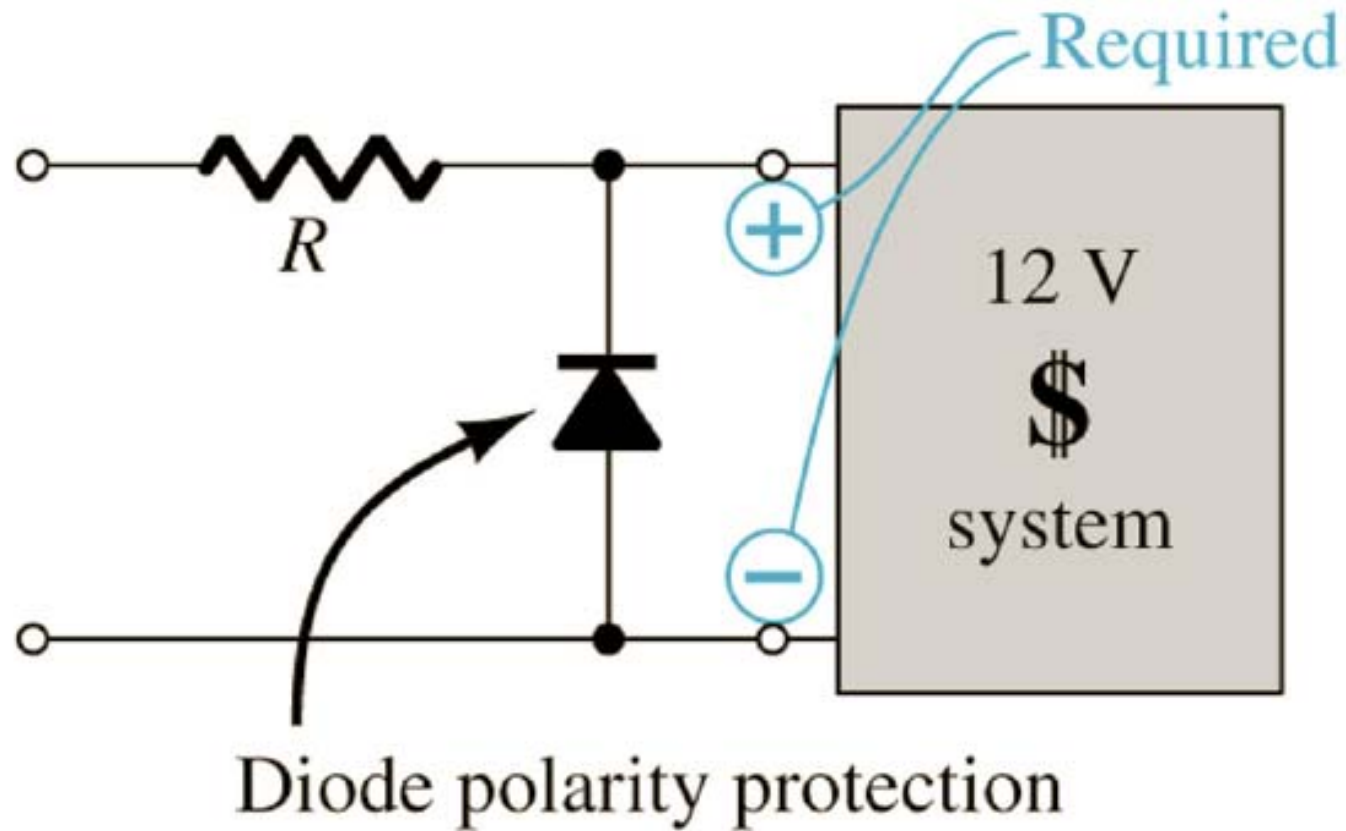


Explique o funcionamento do circuito de proteção contra inversão de polaridade mostrado acima.

# Aplicações simples

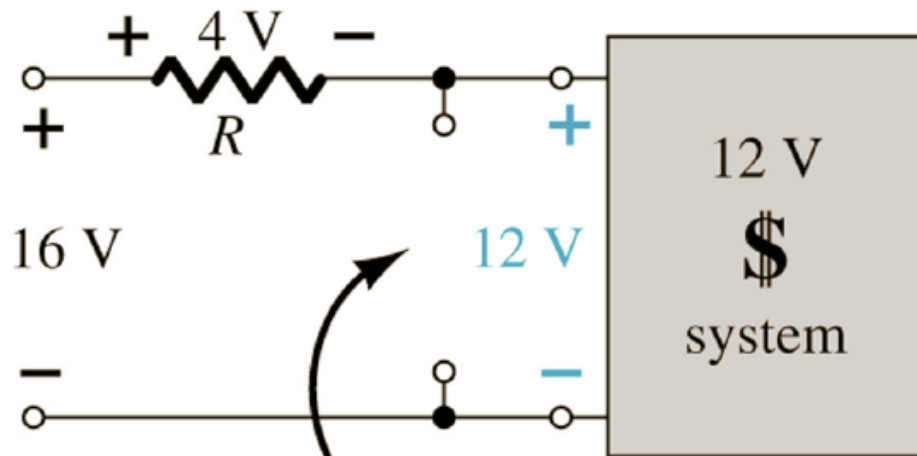

Diode open


Polaridade correta

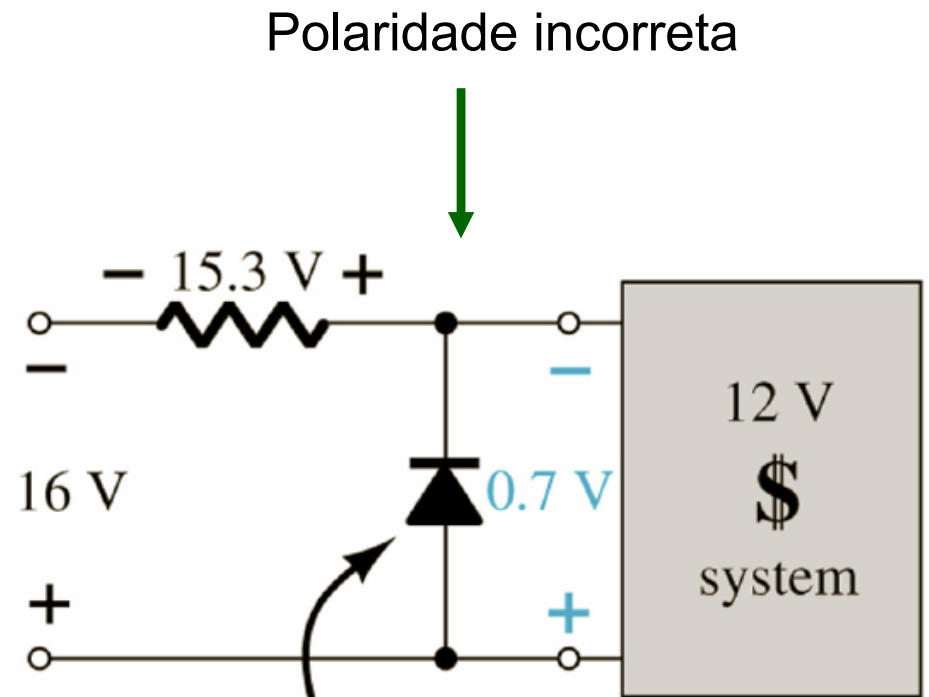

Polaridade incorreta


Diode conducting

## Aplicações simples

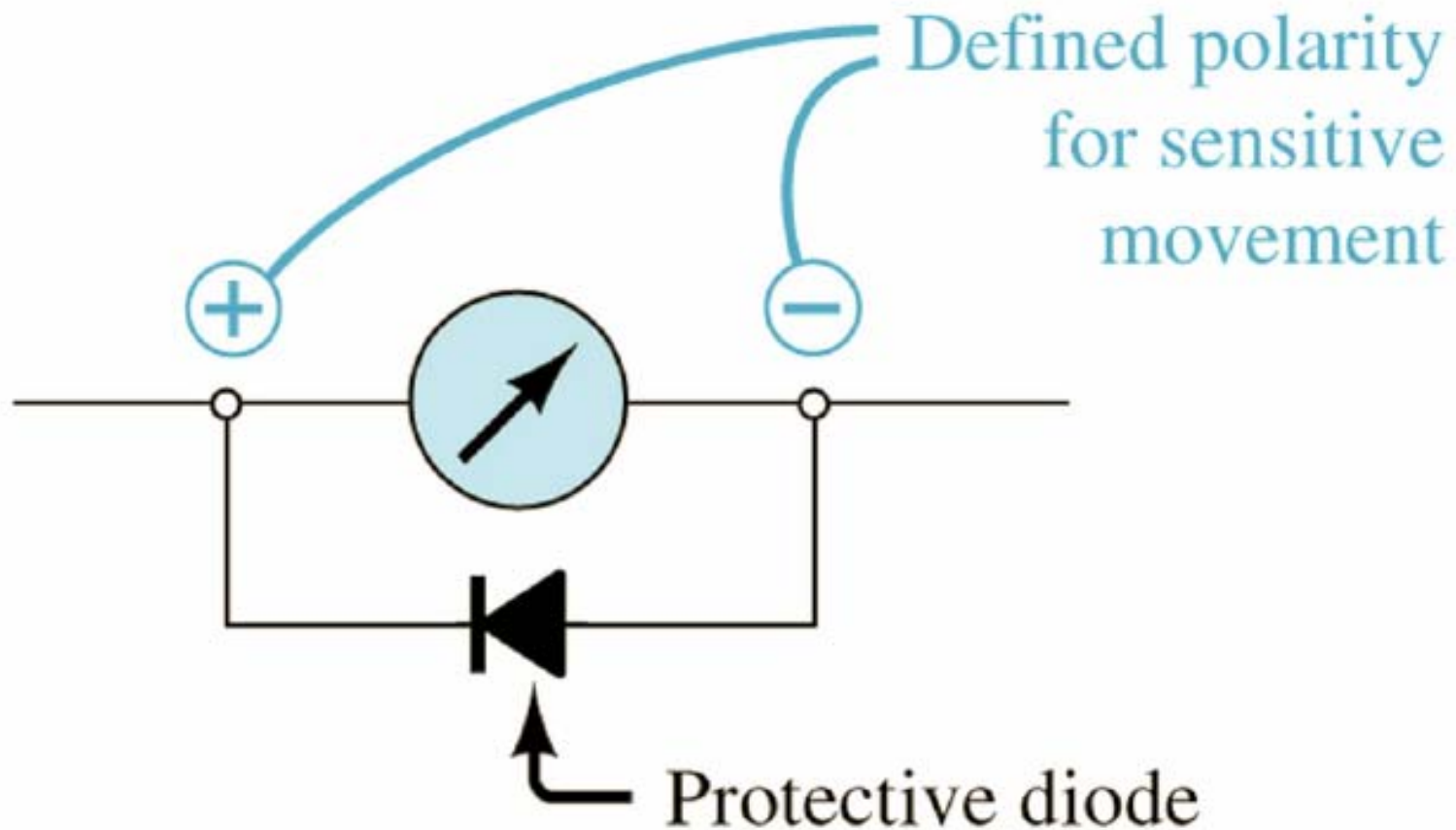

Explique o funcionamento do circuito de proteção de instrumentos sensíveis.

# Aplicações simples

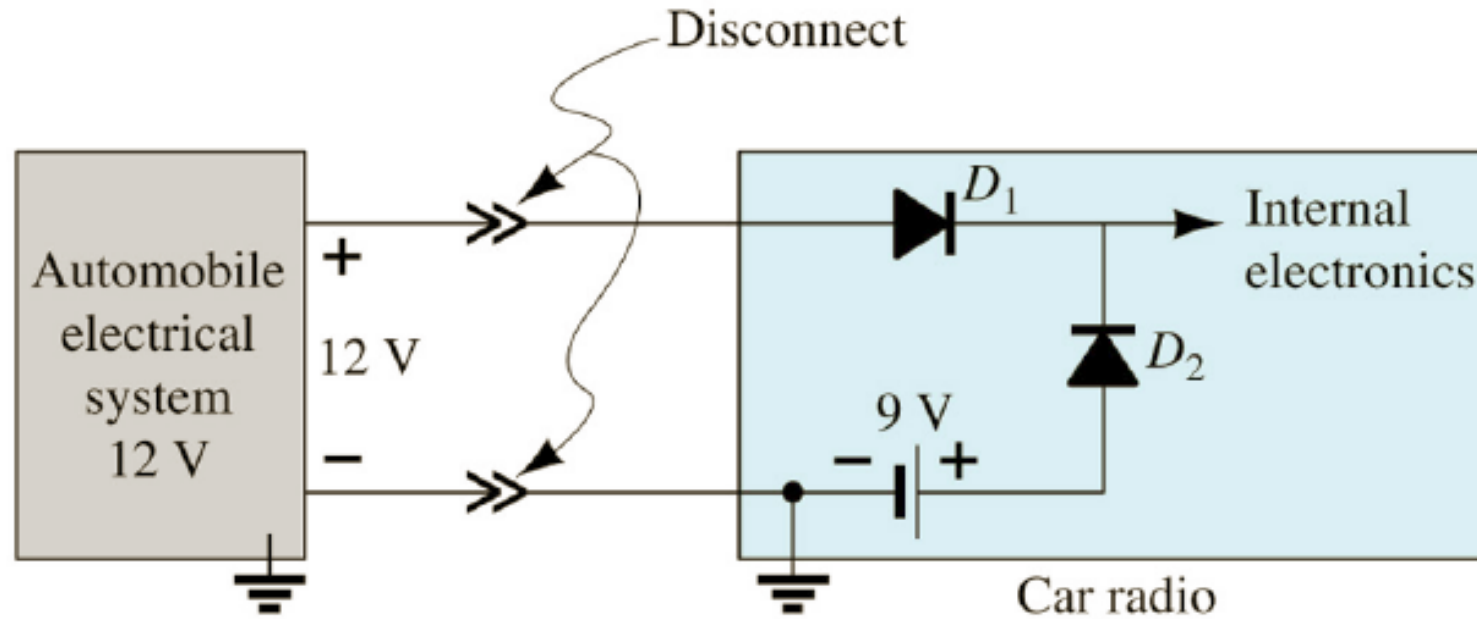

Explique o funcionamento do circuito de backup de memória de auto-rádios.

# Exercícios

---

## **Exercícios selecionados:**

1. Lista capítulo 3 do Malvino;
2. Entre outros ....

# Na próxima aula

---

## **Seqüência de conteúdos:**

1. Análise de circuitos com diodos no laboratório;
2. Identificação de diodos;
3. Testes com diodos.